
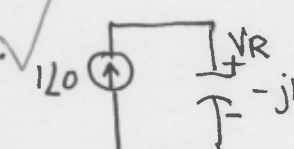
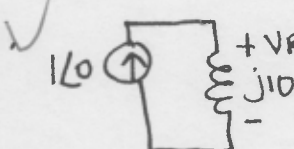
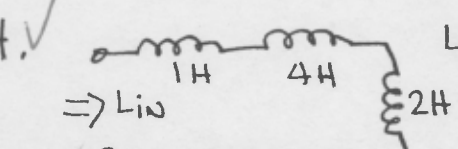



$V = IR =$


1.  $V_R = (a) \frac{1}{10} \angle 0, (b) 10 \angle 90, (c) 10 \angle 0, (d) \frac{1}{10} \angle 45, (e) \frac{1}{10} \angle -45$


2.  $V_R = (a) \frac{1}{10} \angle 90, (b) 10 \angle -90, (c) 10 \angle 90, (d) 10 \angle 45, (e) \frac{1}{10} \angle -90$
 (10) * (10∠-90) = 10∠-90

3.  $V_R = (a) \frac{1}{10} \angle -90, (b) 10 \angle -90, (c) 10 \angle 90, (d) 10 \angle 45, (e) \frac{1}{10} \angle 90$

4.  $L_{in} = (a) \frac{1}{6} H, (b) \frac{1}{7} H, (c) 7H, (d) 0.5H, (e) 0.25H$
 $\Rightarrow L_{in}$

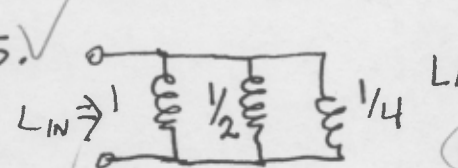
5.  $L_{in} = (a) 1.75H, (b) 7H, (c) \frac{1}{6} H, (d) 6H, (e) \frac{1}{7} H$
 $(1 + 2 + 4)^{-1} = \frac{1}{7} H$

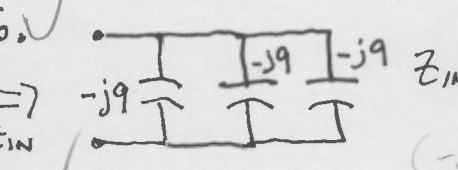6.  $Z_{in} = (a) -27j, (b) 3 \angle -90, (c) \frac{1}{3} \angle -90, (d) 3j, (e) 27 \angle +90$
 $\Rightarrow Z_{in}$
 $(-j \frac{3}{9})^{-1} = 3j$

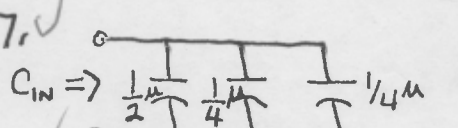
7.  $C_{in} = (a) \frac{1}{10} \mu, (b) 10 \mu, (c) \frac{1}{4} \mu, (d) \frac{1}{2} \mu, (e) 1 \mu$
 $\Rightarrow C_{in}$

8. $V(t) = V_0 \cos 4\pi t$ $f = (a) 4\pi, (b) 4, (c) 2, (d) \frac{1}{4}, (e) \frac{1}{2}$ Hz
 $\omega = 2\pi f \quad 4\pi = 2\pi f \quad f = 2$

9. $V(t) = V_0 \cos 4\pi t$ $T = (a) 4\pi, (b) 4, (c) 2, (d) \frac{1}{4}, (e) \frac{1}{2}$ sec
 $\omega = 2\pi f$

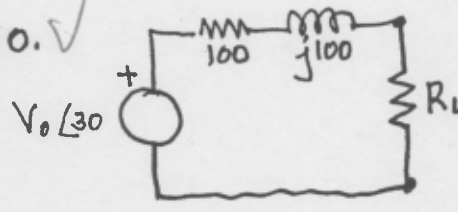10.  $V_0 = 30$
 WHAT VALUE of R_L results in the maximum power delivered to R_L ?
 (a) 100
 (b) $100\sqrt{2}$
 (c) -100
 (d) $-j100$
 (e) 50
 $Z_{eq} = 100 + j100$
 $\sqrt{\omega^2 + \omega^2}$

11. ✓


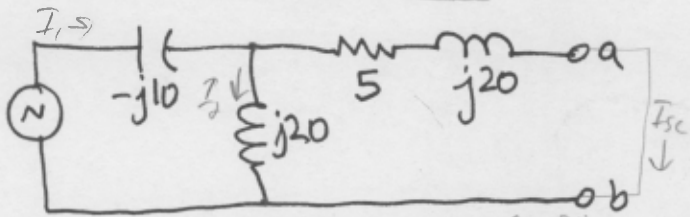


Which of the equivalent circuits shown below is the equivalent of the circuit to the left?


(a) $(\frac{1}{-j10} + \frac{1}{j20})^{-1}$



$80 - 20j - 10j = 80 - 30j$

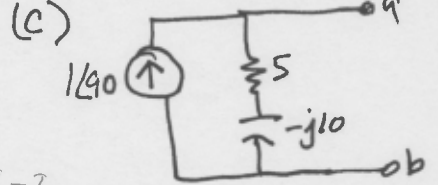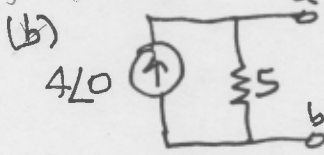

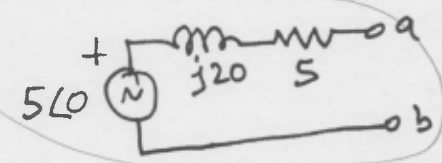(d) $\frac{2j - \frac{1}{20}}{10} = 10\angle 90$




$Z_i = Z_{eq} = -10j$ $I_{sc} = I_1 - I_2$

$I_{sc} = \frac{10\angle 0}{10\angle 90} - \frac{10\angle 90}{5 + j20}$
 $\frac{10}{10\angle 90} - \frac{10\angle 90}{5 + j20}$

$\frac{5\angle 27}{10\angle 65} \angle 283$ (1290)

12. ✓

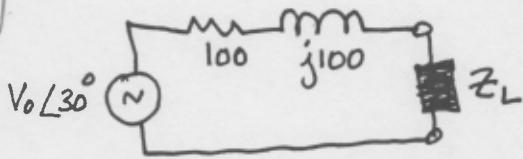

WHAT VALUE of Z_L results in the maximum power delivered to Z_L ?

(a) 100


(b) j100

(c) 100 + j100

(d) -j100

(e) 100 - j100

13. ✓

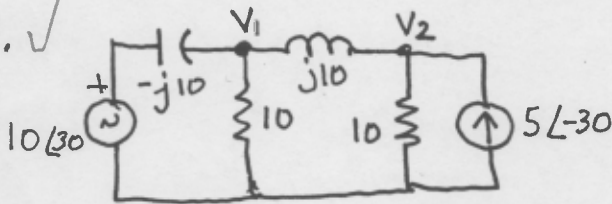

Which of the following is the correct form of the node voltage equations for V_1 and V_2 ?

(a) $\frac{V_1 - 10\angle 30}{10} + \frac{V_1}{-j10} + \frac{V_1 - V_2}{j10} = 0$
 $\frac{V_2 - V_1}{j10} + \frac{V_2}{10} = 5\angle -30$

(b) $\frac{V_1 - 10\angle 30}{\sqrt{-j10}} + \frac{V_1}{10} + \frac{V_1 - V_2}{j10} = 0$
 $\frac{V_2 - V_1}{j10} + \frac{V_2}{10} + 5\angle -30 = 0$


(c) $\frac{V_1 - 10\angle 30}{-j10} + \frac{V_1}{10} + \frac{V_1 - V_2}{j10} = 0$
 $\frac{V_2 - V_1}{j10} + \frac{V_2}{10} - 5\angle -30 = 0$

(d) $\frac{V_1 + 10\angle 30}{-10j} + \frac{V_1}{10} + \frac{V_1 - V_2}{j10} = 0$
 $\frac{V_2 - V_1}{j10} + \frac{V_2}{10} + 5\angle -30 = 0$

(e) $\frac{V_1 - 10\angle 30}{j10} + \frac{V_1}{10} + \frac{V_1 - V_2}{j10} = 0$
 $\frac{V_2 - V_1}{j10} + \frac{V_2}{10} - 5\angle -30 = 0$

Name

14. ✓

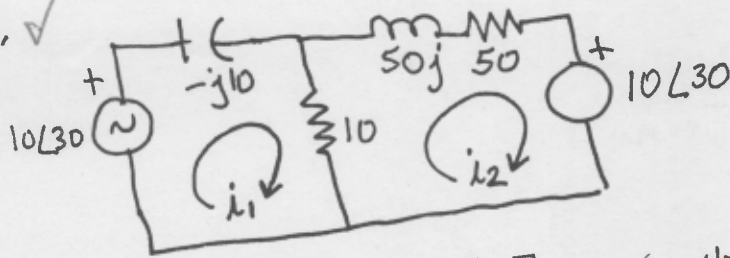

Which of the following is the correct form of the mesh current equations?

$-10\angle 30 - j10i_1 + 10(i_1 - i_2)$
 $10\angle 30 - j + 50j i_2 + 50i_1 + 10\angle 30$

(a) $-10\angle 30 + i_1[-j10] + [i_1 - i_2]10 = 0$ ✓
 $10(i_1 - i_2) + i_2(50 + 50j) + 10\angle 30 = 0$ ✗

(b) $-10\angle 30 - i_1[j10] + [i_1 - i_2] = 0$ ✗
 $10\angle 30 - i_2(50 + 50j) + (i_2 - i_1)10 = 0$

(c) $10\angle 30 + i_1(-j10) + [i_2 - i_1]10 = 0$
 $10\angle 30 + i_2(50 + 50j) + 10(i_2 - i_1) = 0$

(d) $10\angle 30 + i_1(j10) + 10(i_2 - i_1) = 0$ ✓
 $10\angle 30 + i_2(50 + 50j) + 10(i_2 - i_1) = 0$ ✓


(e) $-10\angle 30 + i_1[-j10] + [i_1 - i_2]10 = 0$ ✓
 $(i_2 - i_1)10 + i_2(50 + 50j) = 10\angle 30$ ✗

15. ✓ Current (a) leads, (b) lags, (c) in phase with voltage in a capacitive circuit.

16. ✓ Current (a) leads, (b) lags, (c) in phase with voltage in an inductive circuit.

17. ✓ Current (a) leads, (b) lags, (c) in phase with voltage in a resistive circuit.


18. ✗

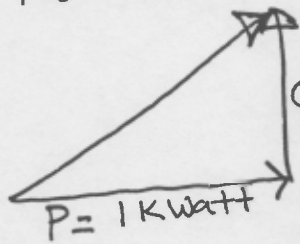

$V = V_0 \cos(\omega t + 15^\circ)$
 $i = I_0 \cos(\omega t + \theta)$ WHAT IS θ ?

- (a) $\theta = 45^\circ$ (b) $\theta = 60^\circ$ (c) $\theta = -45^\circ$
 (d) $\theta = -30^\circ$ (e) $\theta = -15^\circ$

19. ✗

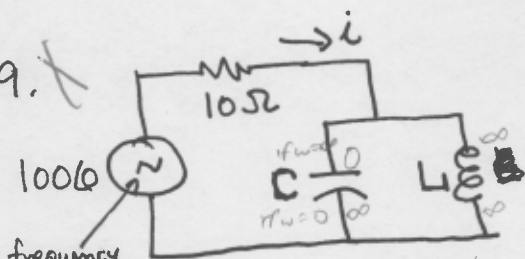

For what value of ω is $i = 0$
 (a) $\omega = 0$, (b) $\omega = LC$ (c) $\omega = \frac{1}{LC}$
 (d) $\omega = \frac{1}{[LC]^{1/2}}$ (e) $\omega = \infty$

frequency = f
 $2\pi f = \omega$

$\frac{1}{0} + \frac{1}{\infty} = 0$ $\frac{1}{\infty} + 0 = 0$
 $I = \frac{V}{Z} = 0$ $Z = \infty$ $10 + \infty = 0$

$[j\omega C + \frac{1}{j\omega L}]^{-1}$
 $\frac{j^2 \omega^2 LC + 1}{j\omega C} + \frac{1}{j\omega C} = \frac{j^2 \omega^2 LC + 1}{j\omega C} + \frac{j\omega L}{j\omega L} = \frac{j^2 \omega^2 LC + 1}{j\omega C} + 1$

20. ✓ RMS of $v(t) = ?$

(a) $\left\{ \frac{1}{T} \int_0^T v(t) dt \right\}^{1/2}$

(b) $\left\{ \frac{1}{T} \int_0^T v^2(t) dt \right\}^{1/2}$ (c) $\left\{ \frac{2}{T} \int_0^{T/2} v^2(t) dt \right\}$

(d) $\left\{ \frac{1}{T} \int_0^T v^{1/2} dt \right\}^2$

(e) $\left\{ \frac{1}{T} \int_0^T v^3 dt \right\}^{1/2}$