

Name


The input to the electrical circuit shown below is voltage  $e_o$ . As a reminder, the impedance equations are

$$i = \frac{\delta e}{R}$$

$$i = \frac{\delta e}{LD}$$

$$i = CD\delta e$$

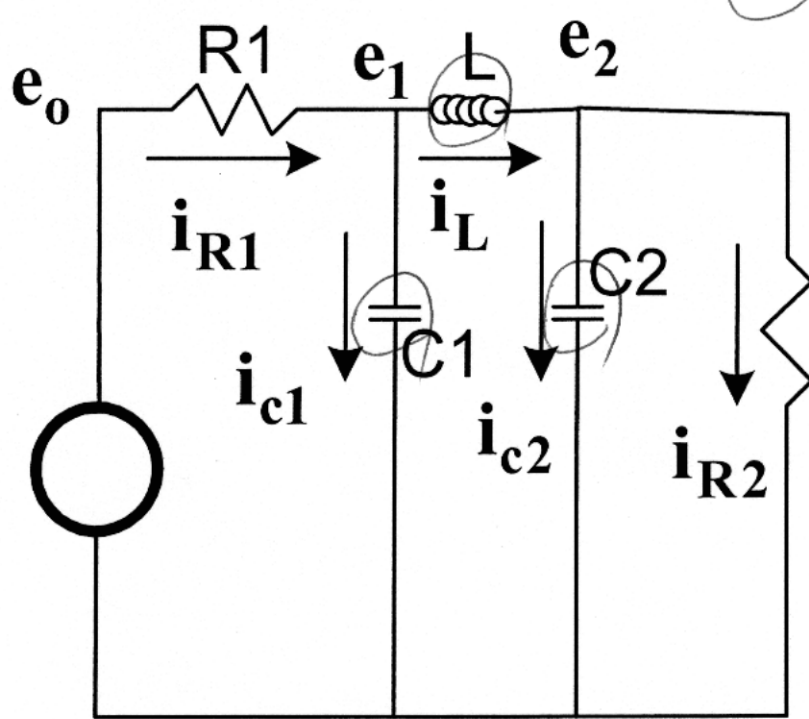To write state variable equations for this circuit, state variables must first be assigned. Assign the state variables for this system.



$x_1 = e_1 = \frac{e_1 - e_2}{LD}$   
 $x_2 = e_2$

$x_1 = e_1$  ; voltage at  $C_1$   
 $x_2 = e_2$  ; " "  $C_2$   
 $x_3 = i_L$  ; current at  $L$   
**R2**

$$i_{R1} = \frac{e_0 - e_1}{R_1} \quad i_{R2} = \frac{e_2}{R_2}$$

$$i_{C1} = C_1 D \cdot (e_1 - 0) \quad i_{C2} = C_2 D (e_2)$$

$$i_L = \frac{e_1 - e_2}{LD}$$