


Lecture 12 & 13

Strain Sensor and Wheatstone Bridge

Announcements

- Reading assignment: p425-p437, p200-207, P441-443, P288-292

Elements of a measurement system

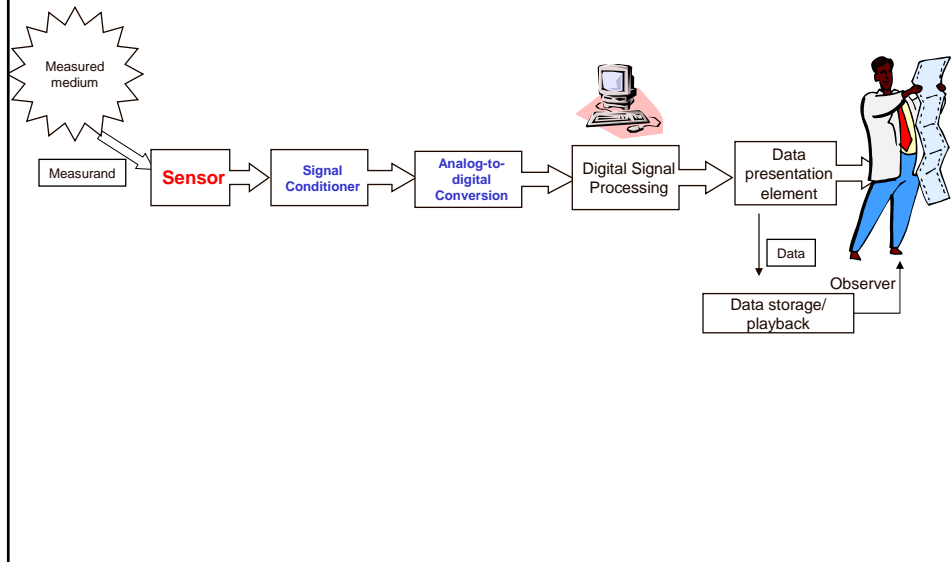


Strain Sensor

- Stress evaluation provides the fundamental understanding of the behavior of load-carrying components
- Experimental measurements are required to verify mechanical design
- Stress can only be measured *indirectly* from strain measurement $\sigma_a = E_m \varepsilon_a$
- Strain definition: $\varepsilon_a = \delta L / L$, $\varepsilon_L = -\nu_p \varepsilon_a$
- Most common strain sensor – Metallic resistance strain gauge


Requirements for Strain Sensor

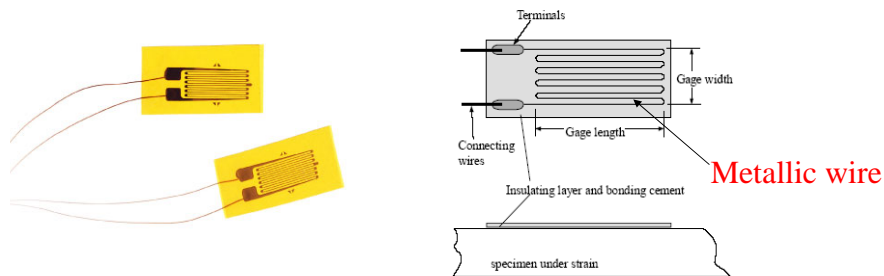- Good spatial resolution
- Unaffected by changes in ambient conditions (temperature, pressure, etc.)
- High-frequency response for dynamic strain measurement



Working Principle of Resistance Strain Gauge

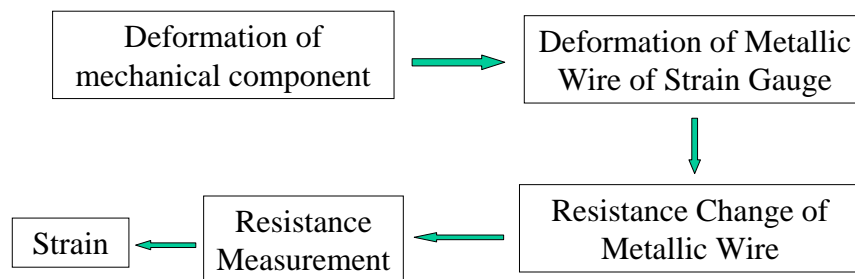- Measure resistance change of a metallic wire



What is the relationship between strain and resistance change?


Strain-Resistance Relationship

$$\delta R/R = (1 + 2\nu_p + \pi_1 E_m) \varepsilon_a = GF * \varepsilon_a$$

GF: Gauge factor


Resistance Measurement

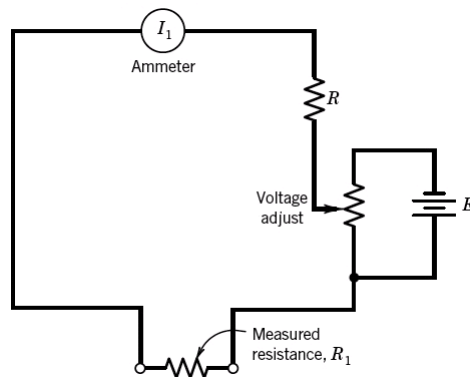- Ohm's Law: $R=U/I$
 - U: voltage
 - I: Current



Wheatstone Bridge

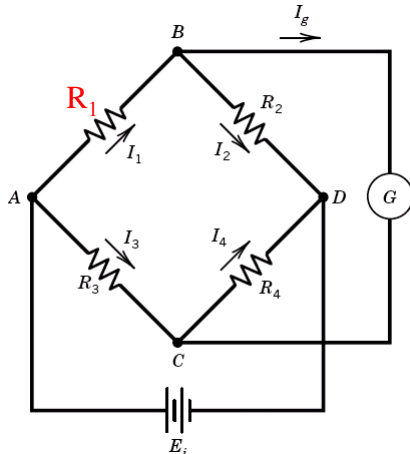- Measure small resistance changes
- R_1 : resistance that changes



Balance conditions:


$$I_g = 0 \rightarrow I_1 = I_2 \text{ and } I_3 = I_4$$

$$\rightarrow R_2/R_1 = R_4/R_3$$

Measuring Methods:

- Null method: adjust one of the resistor to balance the circuit
- Deflection method: measure voltage or current between B and C

Null Method-Strain Gauge

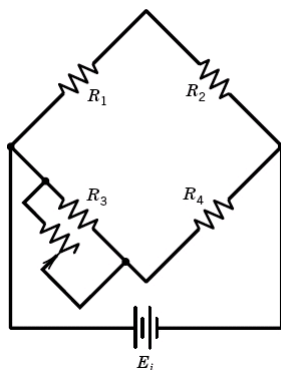

Circuit with a shunt balance

- adjust R_3 to balance the circuit

$$R_2/R_1 = R_4/R_3$$


$$\rightarrow R_1 = R_2 * R_3 / R_4$$

R_3 must be calibrated

$$\delta R_1 / R_1 = GF * \epsilon$$

GF: Gauge Factor

Deflection Method

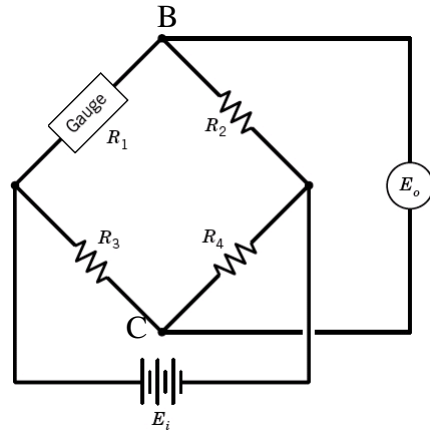



Measure the current or voltage across B and C

$$\delta E_o / E_i = GF/4 * \epsilon$$

Temperature Compensation of Strain Gauge

Temperature sensitivity of strain gauge:

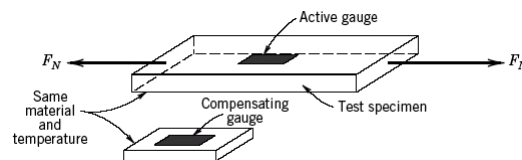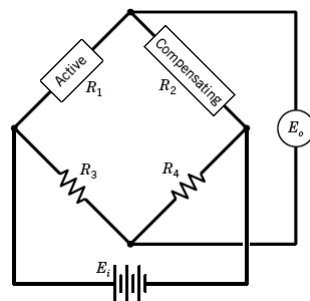- Change in resistivity due to temperature change
- Thermal strain: strain experienced by the gauge due to differential thermal expansion between the gauge and the specimen materials



Active gauge: resistance change due to strain and temperature, $\delta R/R = GF(\epsilon_a + \epsilon_T) \rightarrow \epsilon = \epsilon_a + \epsilon_T$

Compensating gauge: resistance change due to temperature only, $\delta R/R = GF * \epsilon_T \rightarrow \epsilon = \epsilon_T$

Resistance Temperature Detector (RTD)

RTD: a metal wire that exhibits an increase in electrical resistance with temperature:

- $R=R_0[1+\alpha(T-T_0)+\beta(T-T_0)^2+\dots]$
 - R_0 : reference resistance measured at T_0
 - α, β : material constants
- Linear over small temperature range:
 - $R=R_0[1+\alpha(T-T_0)]$
 - α : temperature coefficients of resistivity
- Resistance measurement: Wheatstone bridge